

Bu-Ali Sina University

“ ALU ”

Digital Logic Circuit

Final Project

Dr.Abdoli

Fall 2024

Students : Sahba Mirshahi , Mohammad Matin Soleimani

Student number : 40212358040 40212358021

Design Functions And Their Test Bench

for each function we have input , output and flags (zero , carry , borrow ...)

here is the description of each module and the explanation :

Addition : add two input numbers and produce a result .

the overall view of the module is as follows :

ENTITY Generic_Adder is

 GENERIC (size : INTEGER := 4);

 Port (

 A : IN STD_LOGIC_VECTOR (size-1 downto 0);

 B : IN STD_LOGIC_VECTOR (size-1 downto 0);

 Cin : IN STD_LOGIC ;

 Sum : OUT STD_LOGIC_VECTOR (size-1 downto 0);

 Zero_flag : OUT STD_LOGIC ;

 Carry_flag : OUT STD_LOGIC ;

 Borrow_flag : OUT STD_LOGIC ;

 Overflow_flag : OUT STD_LOGIC ;

 Greater_flag : OUT STD_LOGIC ;

 Equal_flag : OUT STD_LOGIC


);

end Generic_Adder ;

in architecture behavioral of adder we have two signals :

SIGNAL temp_sum : STD_LOGIC_VECTOR (size-1 downto 0);

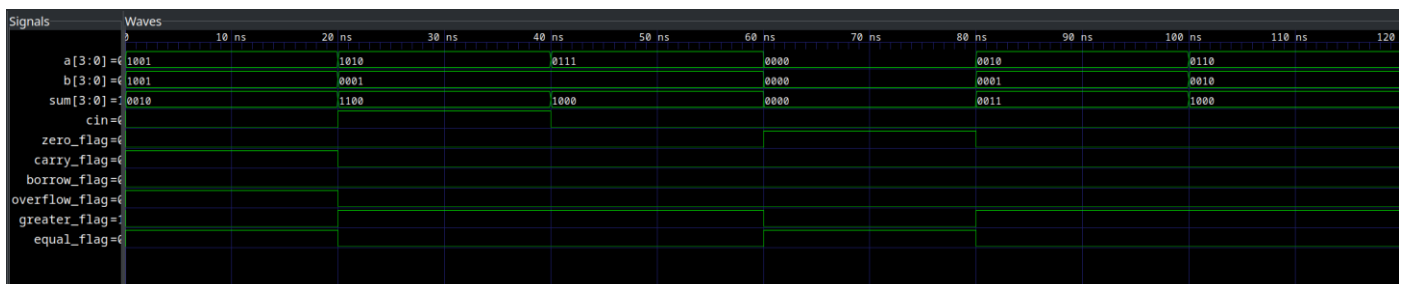SIGNAL Cin_unsigned : unsigned (size-1 downto 0);



Subtraction : subtract one input from the other and produce a result .

the overall view of the module is as follows :

ENTITY Generic_Subtractor IS

 GENERIC (size : integer := 4);

 PORT (

 A , B : IN STD_LOGIC_VECTOR (size - 1 DOWNT0 0);

 Bin : IN STD_LOGIC ;

 Diff : OUT STD_LOGIC_VECTOR (size - 1 DOWNT0 0);

 Zero_flag : OUT STD_LOGIC ;

 Carry_flag : OUT STD_LOGIC ;

 Borrow_flag : OUT STD_LOGIC ;

 Overflow_flag : OUT STD_LOGIC ;

 Greater_flag : OUT STD_LOGIC ;

 Equal_flag : OUT STD_LOGIC

);

END Generic_Subtractor ;

in architecture behavioral of adder we have one signal :

SIGNAL tempSub : STD_LOGIC_VECTOR (size DOWNT0 0);

The signal is created to temporarily compute the general calculations and then assign it to the final answer .

we calculate the result in this way :

tempSub <= STD_LOGIC_VECTOR

(unsigned ('0' & A) - unsigned ('0' & B) - unsigned ('0' & std_logic_vector'(0 => Bin)));

Diff <= tempSub (size - 1 downto 0);

The signal is a (n+1) bit vector , so we should convert all inputs and the carry_in into (n+1) bit vectors . For doing this , we should use AND between the input and '0' .

The amount of flags calculate as follows :

```
Carry_flag <= NOT tempSub ( size );
```

```
Borrow_flag <= tempSub ( size );
```

```
Overflow_flag <= (A(size-1) XOR B(size-1)) AND (A(size-1) XOR tempSub(size-1));
```

Finally , we use the NUMERIC library to compare A and B together and determine greater_than and equality flag .


TestBench : Subtractor

First of all , we should create a signal for each input and output in our module .

to have an easier compile , we write the COMPONENT of the module in the test bench .

After writing the Generic Port and Port Map , we begin the stimulation process . We give A and B desired quantities .

Waveform :

 

NOT : perform a bitwise NOT operation on one input .

the overall view of the module is as follows :

ENTITY generic_not IS

 GENERIC (size : INTEGER := 4);

 PORT (A : IN STD_LOGIC_VECTOR (size-1 DOWNT0 0);

 Result : BUFFER STD_LOGIC_VECTOR (size-1 DOWNT0 0);

 Zero_flag : OUT STD_LOGIC ;

 Carry_flag : OUT STD_LOGIC ;

 Borrow_flag : OUT STD_LOGIC ;

 Overflow_flag : OUT STD_LOGIC ;

 Greater_flag : OUT STD_LOGIC ;


 Equal_flag : OUT STD_LOGIC

);

END generic_not ;

In architecture behavior we have a process to NOT the input A . All flags are zero (they are not applicable in NOT operation) except the Zero_flag .


Waveform :

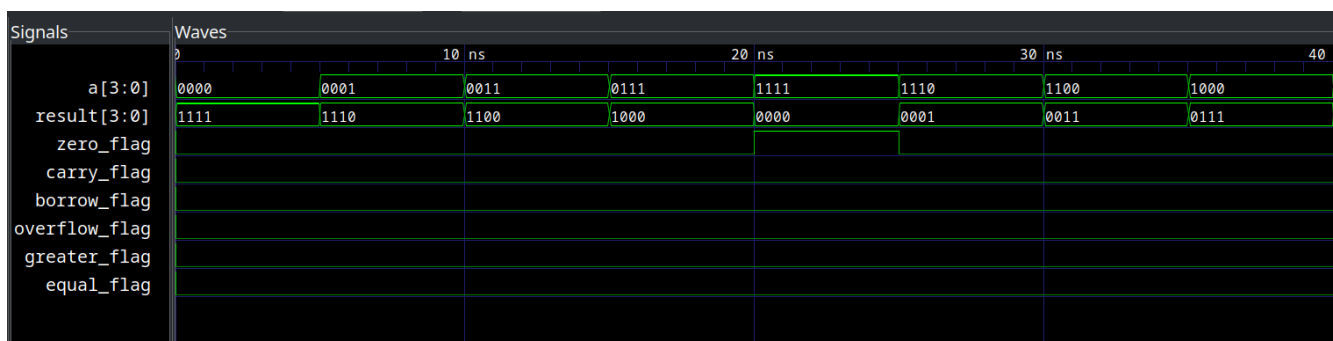

the overall view of the module is as follows :

We check other flags like before .

Waveform :

 

OR : perform a bitwise OR operation on two inputs .

the overall view of the module is as follows :

ENTITY GENERIC_OR IS

 GENERIC (size: INTEGER := 4);

 PORT (

 A : IN STD_LOGIC_VECTOR (size-1 downto 0);

 B : IN STD_LOGIC_VECTOR (size-1 downto 0);

 Result : BUFFER STD_LOGIC_VECTOR (size-1 downto 0);

 Zero_flag : OUT STD_LOGIC ;

 Carry_flag : OUT STD_LOGIC ;

 Borrow_flag : OUT STD_LOGIC ;

 Overflow_flag : OUT STD_LOGIC ;

 Greater_flag : OUT STD_LOGIC ;

 Equal_flag : OUT STD_LOGIC


);

END GENERIC_OR;

In architecture behavior we have a process to OR the input A . Some flags are zero (they are not applicable in OR operation) including carry , borrow and overflow .

We check other flags like before .

Waveform :

 

XOR : perform a bitwise XOR operation on two inputs .

the overall view of the module is as follows :

ENTITY GENERIC_XOR IS

 GENERIC (size: INTEGER := 4);

 PORT (

 A : IN STD_LOGIC_VECTOR (size-1 downto 0);

 B : IN STD_LOGIC_VECTOR (size-1 downto 0);

 Result : BUFFER STD_LOGIC_VECTOR (size-1 downto 0);

 Zero_flag : OUT STD_LOGIC ;

 Carry_flag : OUT STD_LOGIC ;

 Borrow_flag : OUT STD_LOGIC ;

 Overflow_flag : OUT STD_LOGIC ;

 Greater_flag : OUT STD_LOGIC ;

 Equal_flag : OUT STD_LOGIC


);

END GENERIC_XOR ;

In architecture behavior we have a process to XOR the input A . Some flags are zero (they are not applicable in XOR operation) including carry , borrow and overflow .

We check other flags like before .

Waveform :

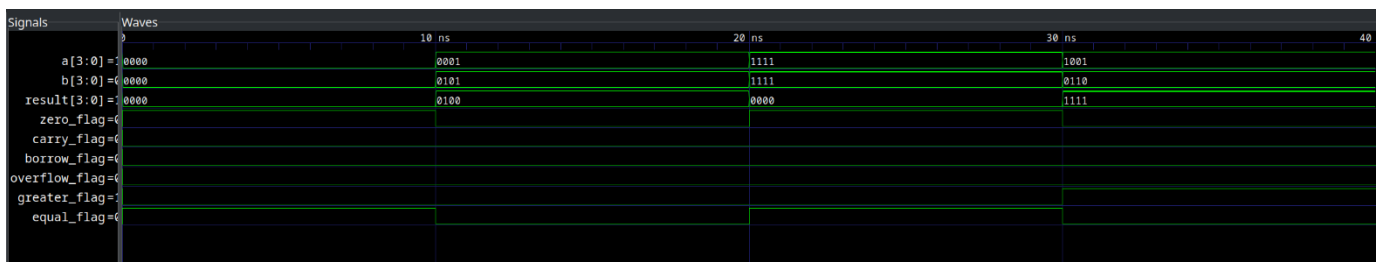

Right Shift : Shift the input bits to the right .

the overall view of the module is as follows :

ENTITY Right_Shift is

 GENERIC (

 size : integer := 4

);

 PORT (

 A : IN STD_LOGIC_VECTOR (size-1 DOWNT0 0);

 Shift : IN STD_LOGIC ;

 Zero_flag : OUT STD_LOGIC ;

 Carry_flag : OUT STD_LOGIC ;

 Borrow_flag : OUT STD_LOGIC ;

 Overflow_flag : OUT STD_LOGIC ;

 Greater_flag : OUT STD_LOGIC ;

 Equal_flag : OUT STD_LOGIC ;


 Result : OUT STD_LOGIC_VECTOR (size-1 DOWNT0 0)

);

END Right_Shift ;

In architecture behavior we have a process to do the right shift and another process to determine the amount of flags .

Waveform :

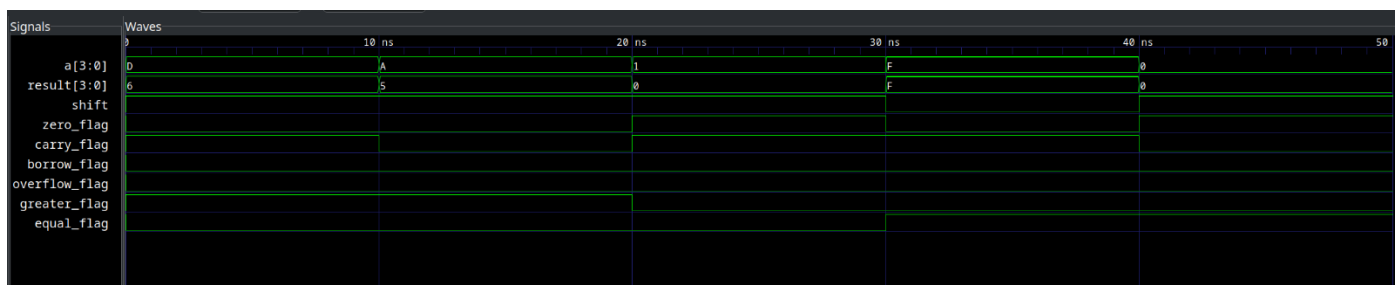

Left Shift : Shift the input bits to the left .

the overall view of the module is as follows :

ENTITY Left_Shift is

GENERIC (

size : integer := 4

);

PORT (

A : IN STD_LOGIC_VECTOR (size-1 DOWNT0 0);

Shift : IN STD_LOGIC ;

Zero_flag : OUT STD_LOGIC ;

Carry_flag : OUT STD_LOGIC ;

Borrow_flag : OUT STD_LOGIC ;

Overflow_flag : OUT STD_LOGIC ;

Greater_flag : OUT STD_LOGIC ;

Equal_flag : OUT STD_LOGIC ;


Result : OUT STD_LOGIC_VECTOR (size-1 DOWNT0 0)

);

END Left_Shift ;

In architecture behavior we have a process to do the left shift and another process to determine the amount of flags .

Waveform :

 

Arithmetic right shift : Shift the input bits to the right , retaining the sign bit for signed operations .

the overall view of the module is as follows :

ENTITY Arithmetic_Right_Shift is

 GENERIC (

 size : integer := 4

);

PORT (

 A : IN STD_LOGIC_VECTOR (size-1 DOWNT0 0);

 Shift : IN STD_LOGIC ;

 Zero_flag : OUT STD_LOGIC ;

 Carry_flag : OUT STD_LOGIC ;

 Borrow_flag : OUT STD_LOGIC ;

 Overflow_flag : OUT STD_LOGIC ;

 Greater_flag : OUT STD_LOGIC ;

 Equal_flag : OUT STD_LOGIC ;


 Result : OUT STD_LOGIC_VECTOR (size-1 DOWNT0 0)

);

END Arithmetic_Right_Shift ;

In architecture behavior we have a process to do the left shift and another process to determine the amount of flags .

Waveform :

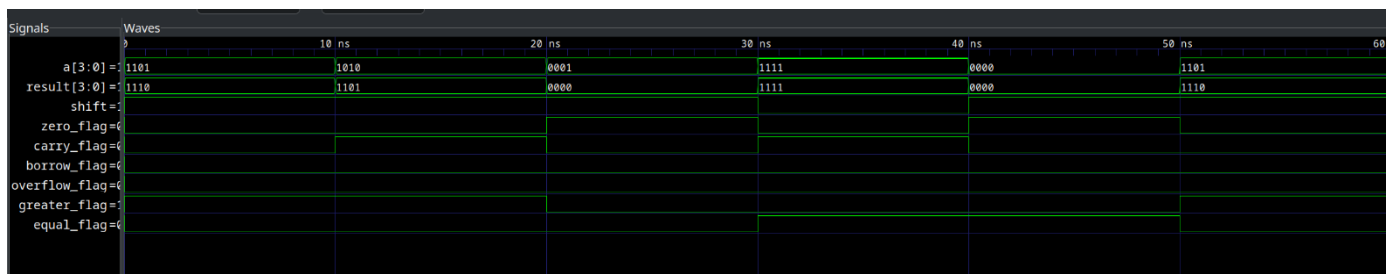

[illegible]

Rotate left : Rotate the bits of the input to the left .

the overall view of the module is as follows :

ENTITY Left_Rotate IS

 GENERIC (size : INTEGER := 4);

 PORT (

 Rotate : IN STD_LOGIC ;

 A : IN STD_LOGIC_VECTOR (size - 1 DOWNTO 0);

 Result : OUT STD_LOGIC_VECTOR (size - 1 DOWNTO 0);

 Zero_flag : OUT STD_LOGIC ;

 Carry_flag : OUT STD_LOGIC ;

 Borrow_flag : OUT STD_LOGIC ;

 Overflow_flag : OUT STD_LOGIC ;

 Greater_flag : OUT STD_LOGIC ;


 Equal_flag : OUT STD_LOGIC

);

END Left_Rotate ;

In architecture behavior we have a process to do the right rotate and another process to determine the amount of flags . we use a signal to save the temp result and assign it to result at the end .


Waveform :

 

for these two modules we just have two inputs (A and B) and a result .


Comparison : Output 1 if input A is greater than input B ; otherwise , output 0 .

Waveform :

 

Equality check : Output 1 if input A is equal to input B ; otherwise , output 0 .

Waveform :

 

Test benches : in all test benches we define a COMPONENT .
make an instance and port it to our desired module .

Control Unit

in this ENTITY we control all operations . we have an input named Opcode that shows the operation number .

for example if Opcode = "0001" the control unit do addition between the inputs A and B and so on ...

first of all we should write all COMPONENTS that we designed before .
after that , we make 13 instances for each operation (Add , Sub , And ...)
and port them to their module .

Test Bench :

In the test bench we write one test case for each operation .